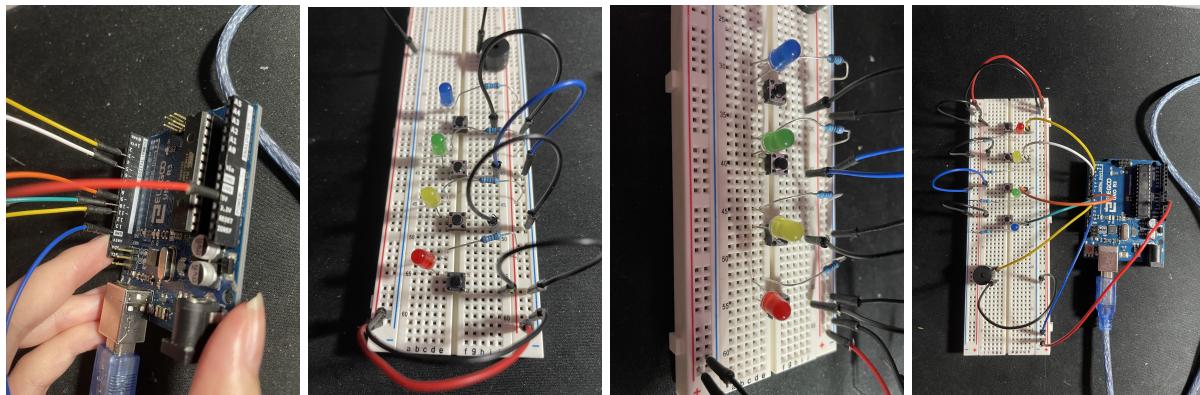

Etude 3: Mind-It

part one

photos



notes

Started with inserting the wires on the bread board and the Arduino piece separately

Noticed the structure of the board:

- The buttons linked to the LED (diode) goes to ground terminal (-)
- The LED (anode) links to a resistor that goes to positive terminal (+)
- Buzzer connects to Digital Input number 11

When connecting the two pieces (board + arduino), I linked each LED (diode) to its designated Digital Input number (Blue = 10 , Green = 9 , Yellow = 5, Red = 3)

